

Sam Wisnoski

Introduction to Sensors, Instrumentation, and Measurement

02/22/2024


Lab Four: Using Capacitors to Measure Humidity

Purpose:

Build a circuit to measure relative humidity by sensing capacitance of the sensor.


Results:

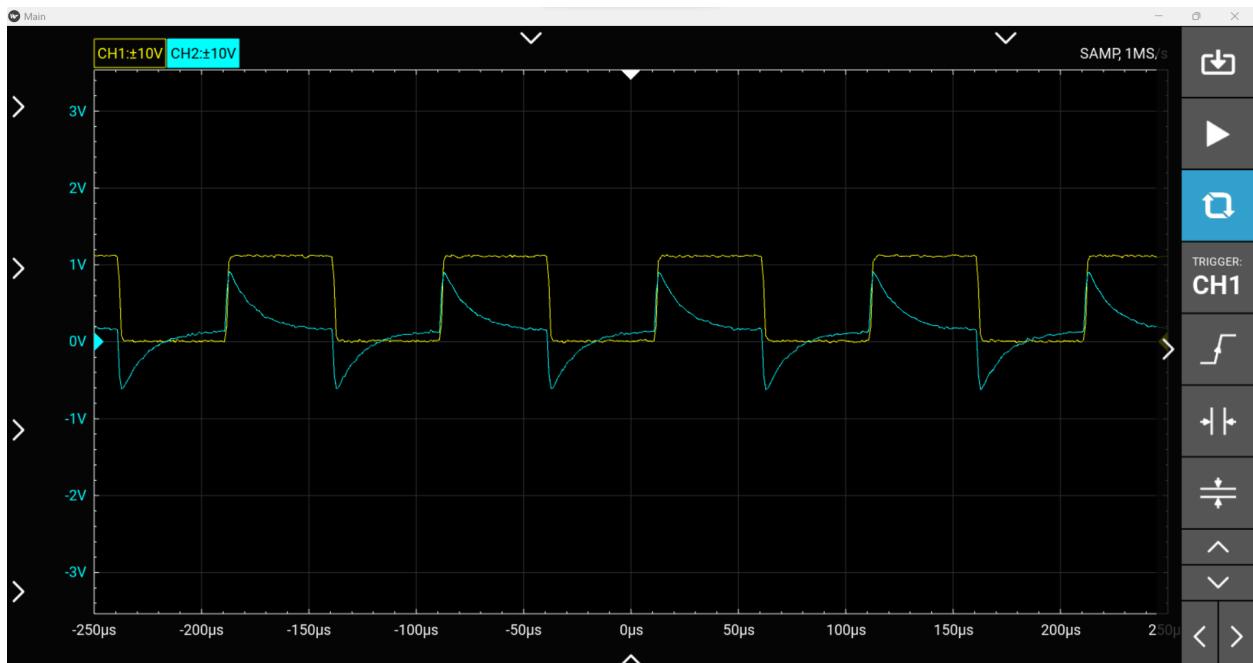- 1.) Screenshot of circuit output for a couple of cycles with a caption




Graph of Time (microseconds) vs. Voltage (V) of a CR circuit (120 picofarads and 100kΩs). The input is a square wave from 0 volts to 1 volt with a frequency of 10k Hz. Channel one (yellow) is taken over the entire circuit, while channel two (blue) is taken over just the second resistor.

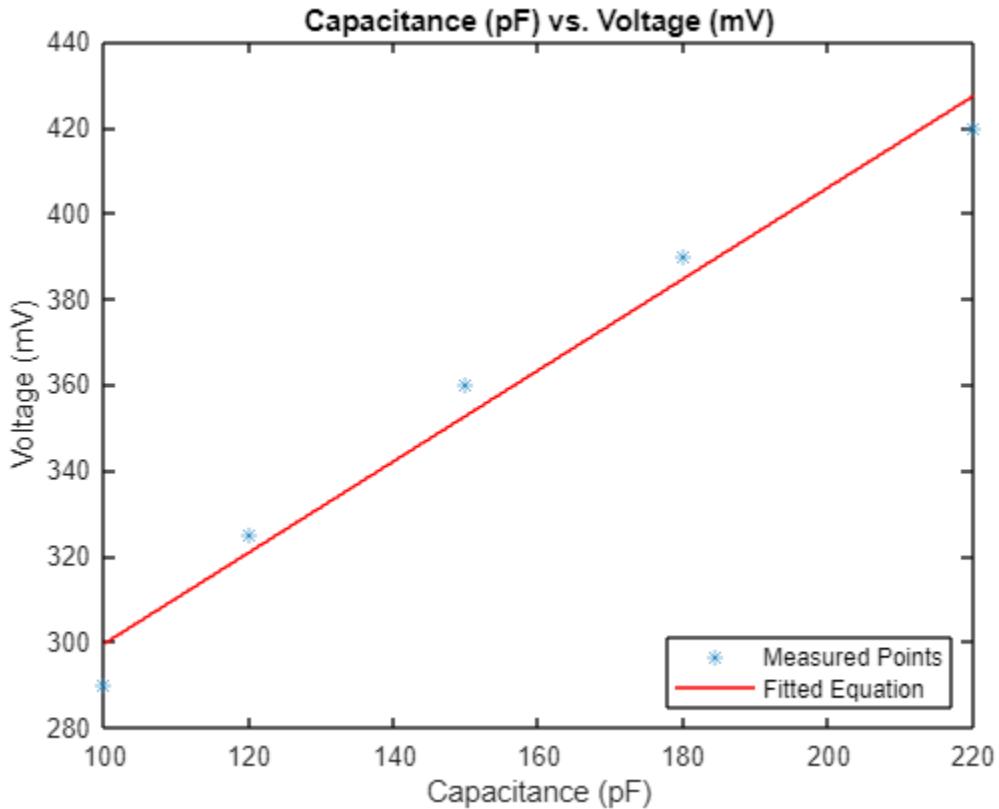- 2.) Circuit calibration curve with labeled axes and units, fitted equation to the data, and caption.



Calibration curve for Voltage (mV) vs Capacitance (pF) in a CR circuit. The input was a square wave from 0 volts to 1 volt with a frequency of 10k Hz. The voltage was a V-RMS reading taken over a 100kΩ resistor. The fitted equation is: $\text{Capacitance} = (\text{Voltage} - 193.0373)/1.0647$.

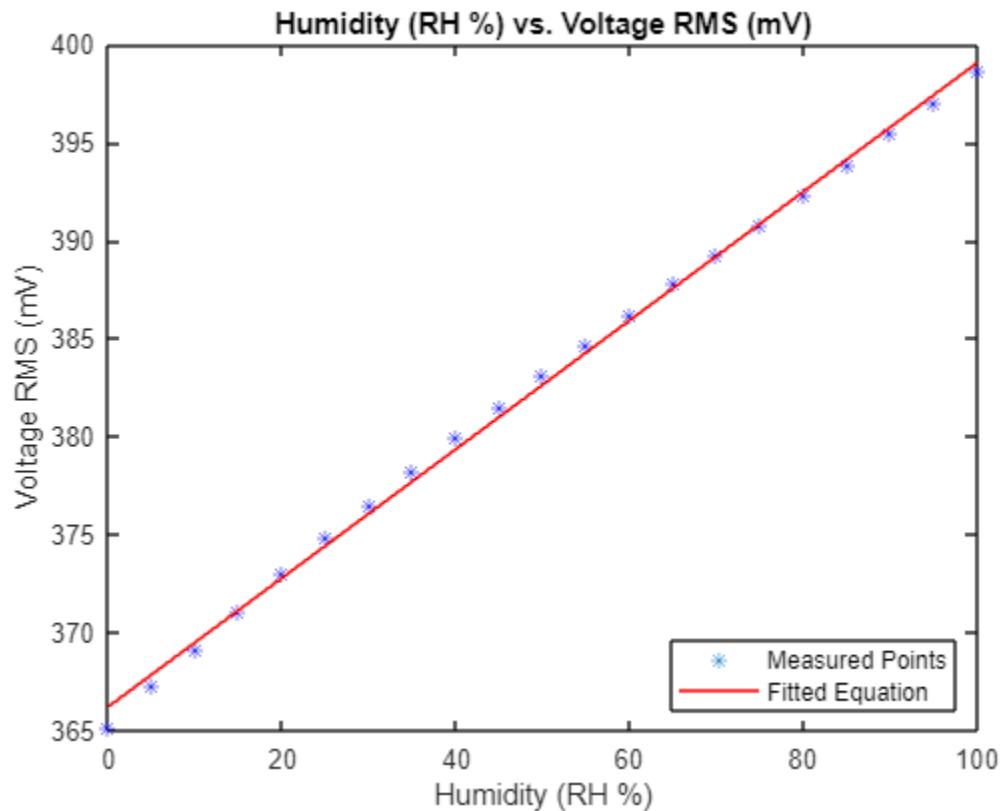3.) Measurement curve with labeled axes, units, and caption.



*Measurement curve for Voltage (mV) vs Humidity (RH %) in a circuit with a humidity sensor and a 100kΩ ohm resistor. The humidity vs capacitance data is sourced from this [humidity data source](#). The capacitance is then converted to voltage based on the voltage equation Capacitance = (Voltage - 193.0373)/1.0647 from the graph above. The fitted equation for this graph is: **Voltage = 0.3286 * Humidity + 366.2027**.*

4.) Measurement of % relative humidity and reflections on whether it is a reasonable result.

The humidity sensor, when plugged into my circuit under the same conditions as the capacitors, had a reading of ~385 mV. When plugged into the transfer equation:

$$Voltage = 0.3286 * Humidity + 366.2027.$$



$$Humidity = (Voltage - 366.2027) / 0.3286$$

$$Humidity = (385 - 366.2027) / 0.3286$$

$$Humidity = 57.2041996\%$$

This is a reasonable result when compared to the humidity reading for the Needham area at the same time: 49% (as measured by www.weather.com).

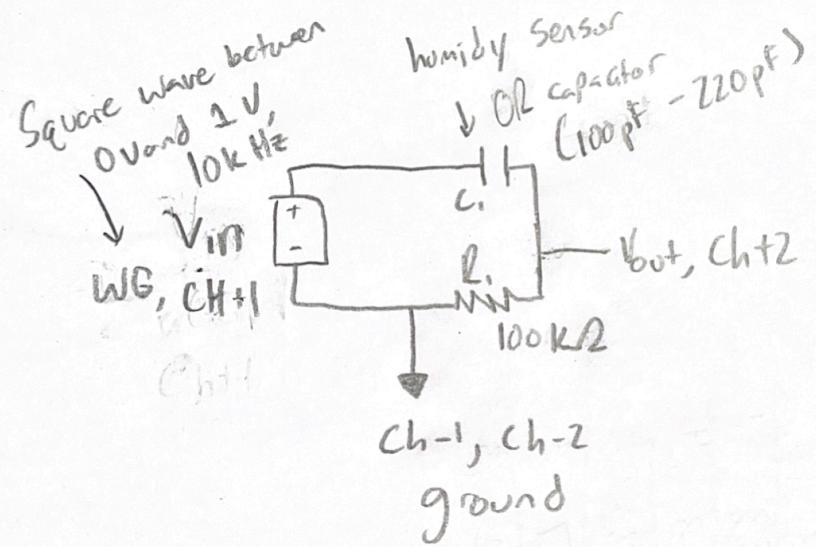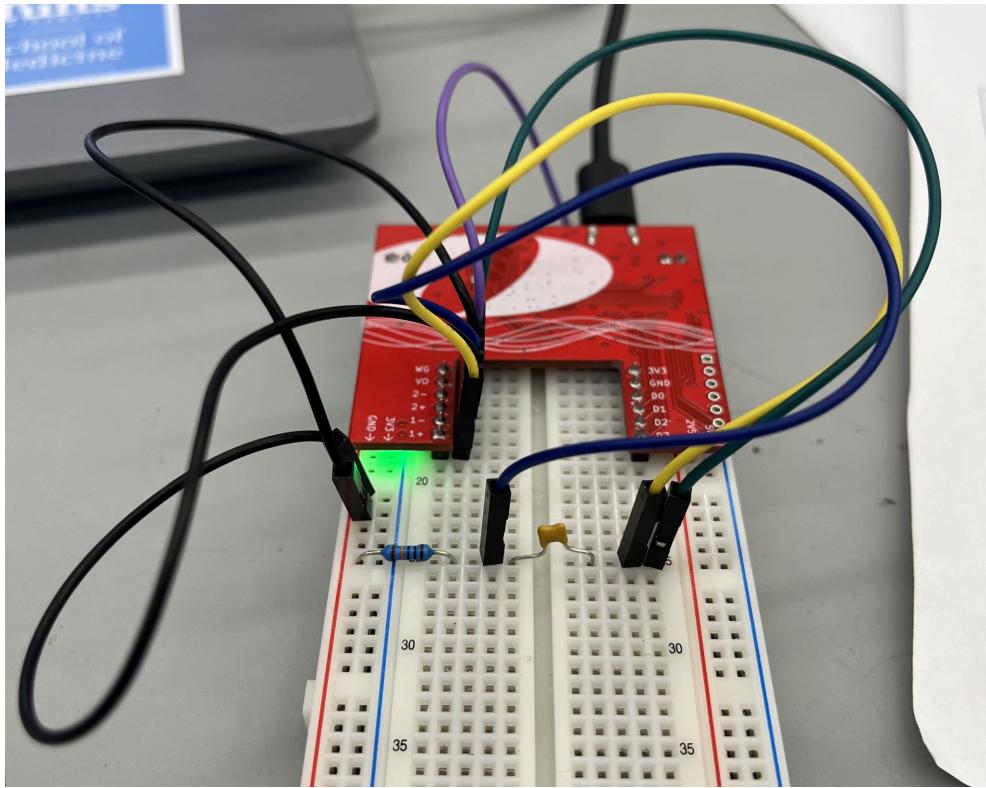5.) A sketch of circuit with labeled components and O-scope connections with a photo.



6.) Your code or screenshot of equations used for Excel.

```
clear; % clear the memory
clf; % clear the figure to start new

Capacitance = [100; 120; 150; 180; 220];
Voltage = [290; 325; 360; 390; 420];

plot(Capacitance,Voltage,'*'); % plot data as * points
hold on; % hold the plot so that the next one will overlay

p = polyfit(Capacitance,Voltage,1); % p returns 2 coefficients fitting r = a_1 * x + a_2
r = p(1) .* Capacitance + p(2); % compute a new vector r that has matching datapoints in x
% line of best fit: Voltage = 1.0647 * Capacitance + 193.0373
% to convert voltage to capacitance: Capacitance = (Voltage - 193.0373)/1.0647

plot(Capacitance, r,'r')

title("Capacitance (pF) vs. Voltage (mV)")
xlabel('Capacitance (pF)')
ylabel('Voltage (mV)')
legend("Measured Points", "Fitted Equation", "Location", "southeast")
hold off

Humidity = [0; 5; 10; 15; 20; 25; 30; 35; 40; 45; 50; 55; 60; 65; 70; 75; 80; 85; 90; 95; 100];
Capacitance = [161.6; 163.6; 165.4; 167.2; 169.0; 170.7; 172.3; 173.9; 175.5; 177.0; 178.5; 180;
181.4; 182.9; 184.3; 185.7; 187.2; 188.6; 190.1; 191.6; 193.1];
%Voltage = 1.0647 * Capacitance + 193.0373
Cap_to_Voltage = 1.0647 .* Capacitance + 193.0373;

plot(Humidity,Cap_to_Voltage,'*', 'Color','blue'); % plot data as * points
hold on; % hold the plot so that the next one will overlay

p_new = polyfit(Humidity,Cap_to_Voltage,1); % p_new returns 2 coefficients fitting r = a_1 *
x + a_2
r_new = p_new(1) .* Humidity + p_new(2); % compute a new vector r_new that has matching
datapoints in x
% line of best fit: Voltage = 0.3286 * Humidity + 366.2027
% to convert voltage to capacitance: Humidity = (Voltage - 366.2027)/0.3286

plot(Humidity, r_new,'r')
title("Humidity (RH %) vs. Voltage RMS (mV)")
xlabel('Humidity (RH %)')
ylabel('Voltage RMS (mV)')
legend("Measured Points", "Fitted Equation", "Location", "southeast")
```