

Sam Wisnoski

Introduction to Sensors, Instrumentation, and Measurement

03/17/2024


Lab Seven: Pulse measurement with light


**Purpose:**

Design an oximeter using a photodiode, filters and op-amps.

**Results:**

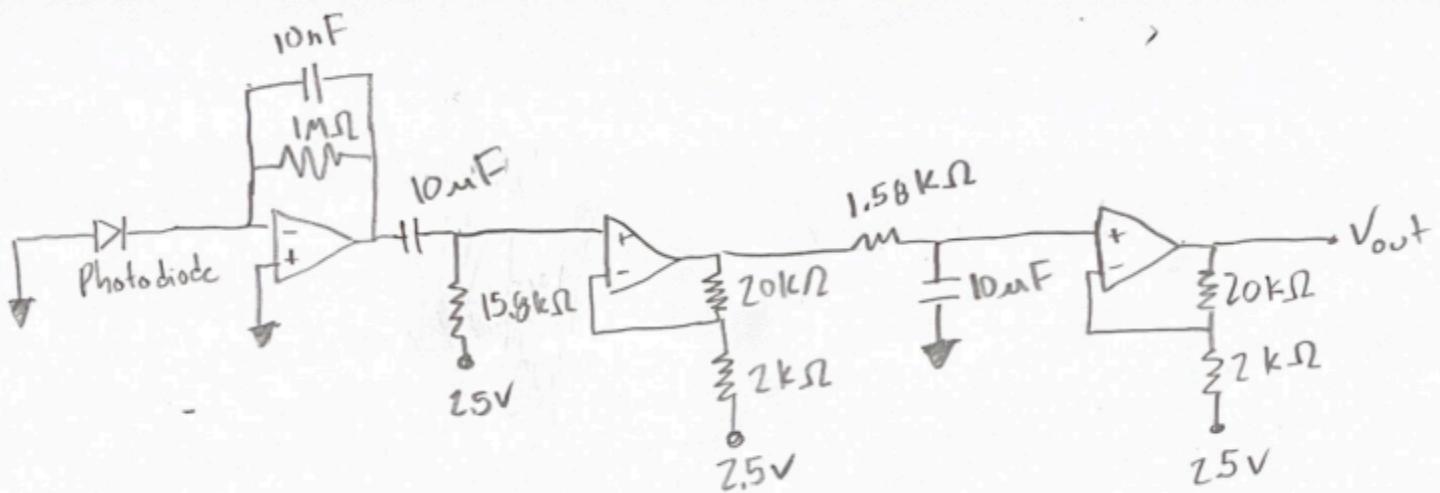- 1.) 1 point: Your final circuit schematic with labeled component values and a photo of your circuit. Sketch the circuit so someone else could build the circuit from your drawing.



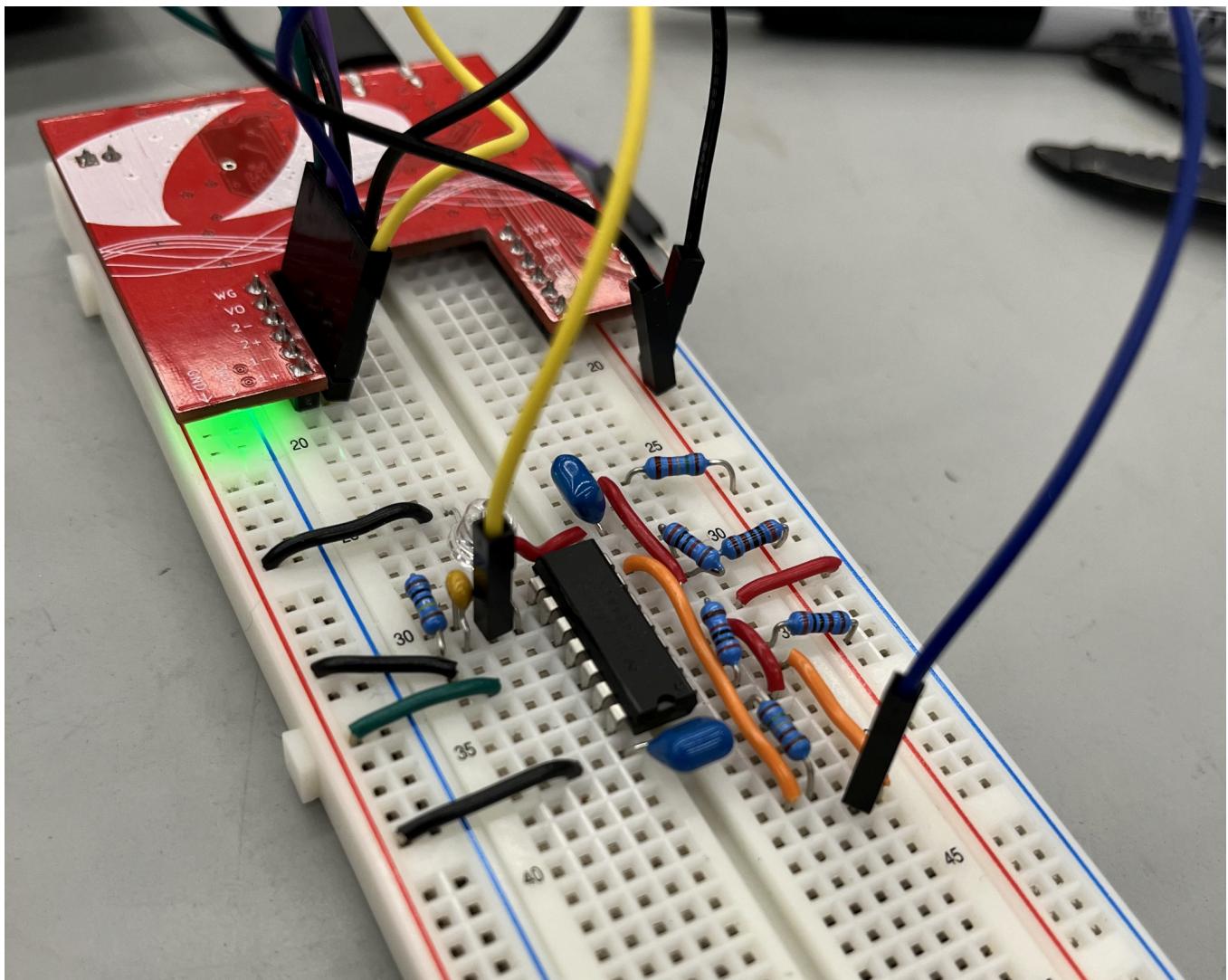

2.) 1 point: A short explanation that shows how you selected resistor and capacitor values with calculations.

There were four separate parts of the circuit that I needed to calculate capacitor and resistor values for: high-pass filter with cutoff frequency of 1Hz, low-pass filter with cutoff frequency of 10Hz, and two op-amps with a gain of ~10. For the two op-amps, I chose values of  $20\text{k}\Omega$  and  $2\text{k}\Omega$  to ensure that the op-amp wouldn't require more than 20 mA of current ( $V/(R_1+R_2)$  can't be higher than 20mA).

a.) high-pass filter with cutoff frequency of 1Hz:

$$\begin{aligned} \text{cutoff frequency} &= 1/(2*\pi*R*C) \\ 1\text{Hz} &= 1/(2*\pi*RC) \\ R*C &= 1/(2*\pi) = 0.158 \\ \text{If we choose } C &= 10\mu\text{F}, \text{ then } R \text{ must be } R = 15.8\text{k}\Omega \end{aligned}$$

b.) low-pass filter with cutoff frequency of 10Hz:


$$\begin{aligned} \text{cutoff frequency} &= 1/(2*\pi*R*C) \\ 10\text{Hz} &= 1/(2*\pi*RC) \\ R*C &= 1/(2*\pi) = 0.0158 \\ \text{If we choose } C &= 10\mu\text{F}, \text{ then } R \text{ must be } R = 1.58\text{k}\Omega \end{aligned}$$

c.) two op-amps with a gain of ~10

$$\begin{aligned} \text{gain} &= R_1/R_2 + 1 \\ 11 &= R_1/R_2 + 1 \\ R_1/R_2 &= 10 \\ \text{If we choose } R_1 &= 20\text{k}\Omega, \text{ then } R_2 \text{ must be } R_2 = 2\text{k}\Omega \end{aligned}$$

3.) 1 point: Measured cutoff frequencies and amplifier gains for your full circuit (a Bode plot will do).


Bode Plot for Photodiode Circuit

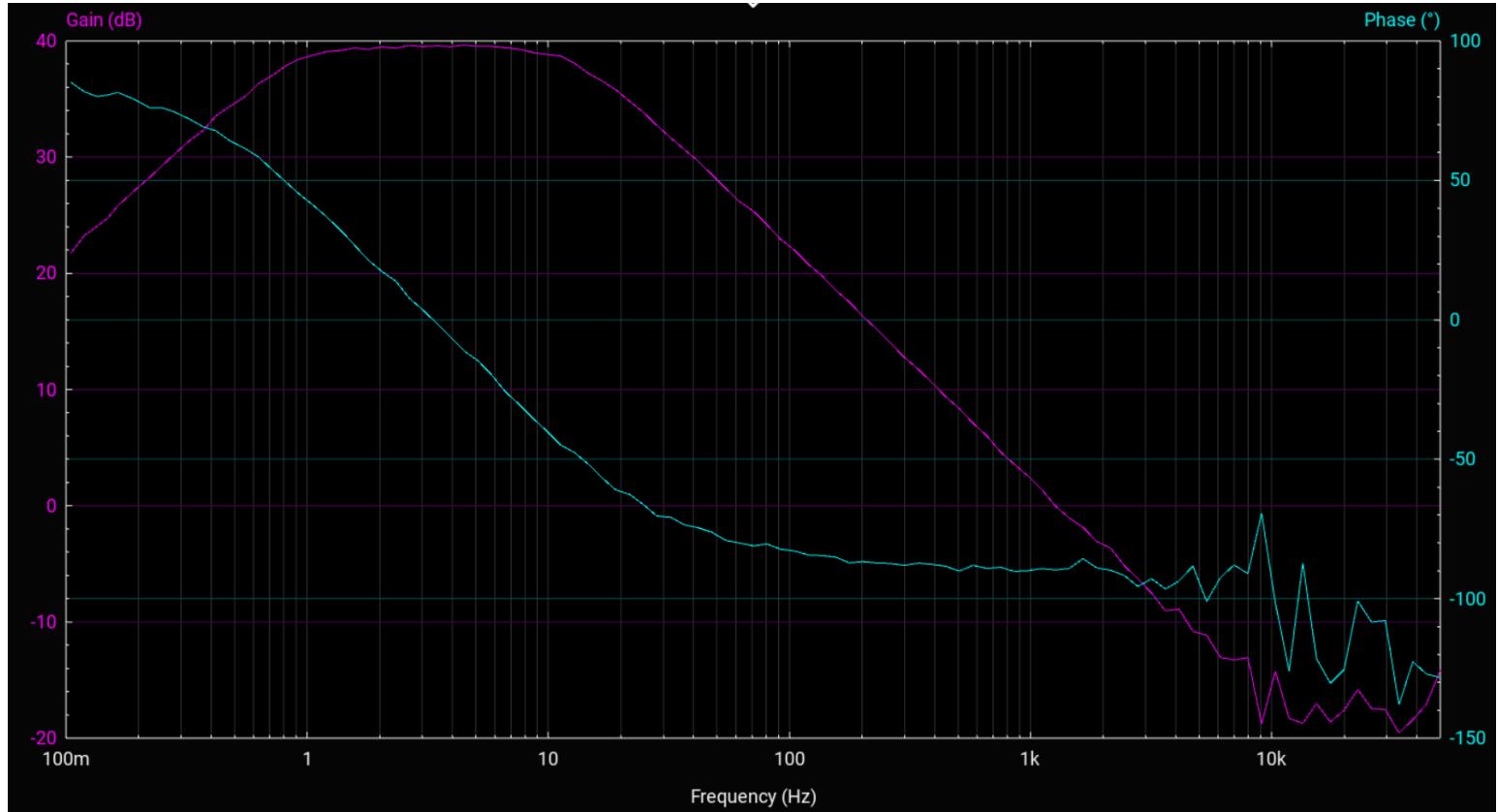

*This circuit contains a high-pass filter with a cutoff frequency of 1Hz, a op-amp with a gain of 11, a low-pass filter with a cutoff frequency of 10Hz, and a second op-amp with a gain of 11. In the plot, you can clearly see the gain at a max between frequencies of 1Hz and 10Hz. The Bode Plot was run with an amplitude of 16.59 mV between 100mHz and 50kHz.*

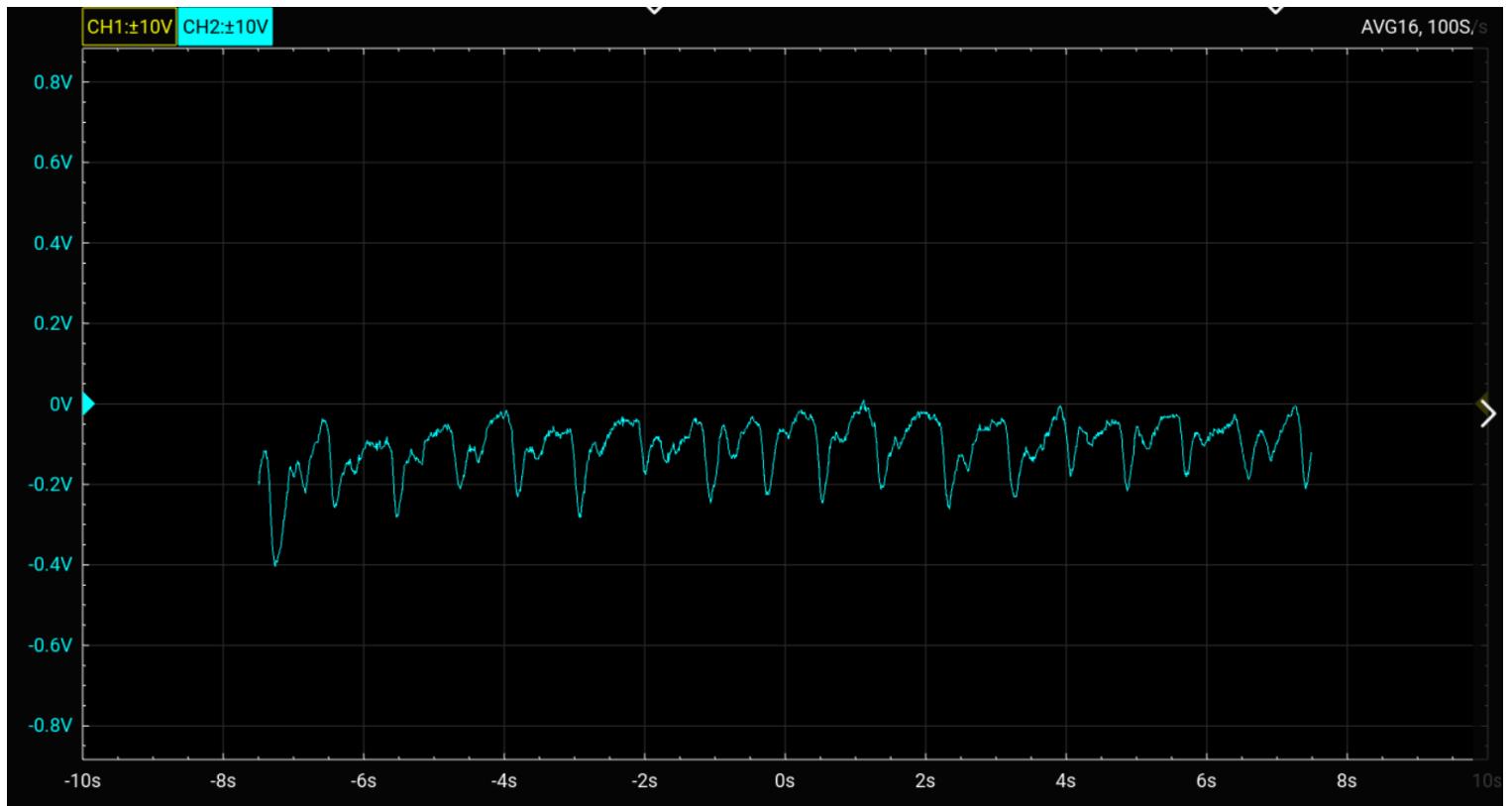- 4.) 1 point: Clean scope trace of your pulse with this circuit (screenshot is fine) with a caption.

Trace of my Pulse (measured with voltage over time)



*My pulse is measured using a photodiode. The photodiode and integrated circuit measures the variation in light through my finger in the 1 Hz to 10 Hz range (using a high-pass and low-pass filter), then amplifies that variation by 121 through two op-amps with gains of 11. In the graph, each dip in voltage is a heartbeat, since the increased amount of blood in my finger blocks the light.*